

Learning Objective 1.4: I can calculate input impedance, feed considerations, and the role of baluns in an antenna feed system.

Show your work. A **Documentation** line at the end is required (write **None** if you did not collaborate).

1. **Radiation resistance and efficiency.** A short dipole has length $\ell = 0.08\lambda$. Its conductors contribute a loss resistance of $R_{\text{loss}} = 1.5 \, \Omega$.

(a) Compute the radiation resistance $R_{\text{rad}} = 80\pi^2(\ell/\lambda)^2$.

$$R_{\text{rad}} = 80\pi^2(0.08)^2 = 789.6 \times 0.0064 \approx 5.05 \, \Omega$$

$$R_{\text{rad}} = \boxed{\approx 5.05 \, \Omega}$$

(b) Compute the radiation efficiency η_{rad} .

$$\eta_{\text{rad}} = \frac{R_{\text{rad}}}{R_{\text{rad}} + R_{\text{loss}}} = \frac{5.05}{6.55} \approx 0.77$$

$$\eta_{\text{rad}} = \boxed{\approx 0.77 \, (77\%)}$$

(c) The short dipole's directivity is $D = 1.5$ (1.76 dBi). Find the gain in dBi.

$$G_{\text{dBi}} = 1.76 + 10\log_{10}(0.77) = 1.76 - 1.13 \approx 0.6 \, \text{dBi}$$

$$G = \boxed{\approx 0.6 \, \text{dBi}}$$

2. Feeding a half-wave dipole with 50 Ω coax.

- (a) A dipole trimmed to resonance presents $Z_{\text{in}} = 70 + j0 \Omega$. Find Γ , VSWR, return loss, and mismatch loss on a 50 Ω line.

$$\begin{aligned}\Gamma &= \frac{70 - 50}{70 + 50} = 0.167 \\ \text{VSWR} &= \frac{1.167}{0.833} \approx 1.40 \\ \text{RL} &= -20\log_{10}(0.167) \approx 15.6 \text{ dB} \\ L_{\text{mm}} &= -10\log_{10}(1 - 0.167^2) \approx 0.12 \text{ dB}\end{aligned}$$

$$\Gamma = 0.167 \text{ (unitless)}$$

$$\text{VSWR} = \approx 1.40$$

$$\text{RL} = \approx 15.6 \text{ dB}$$

$$L_{\text{mm}} = \approx 0.12 \text{ dB}$$

- (b) An *untrimmed* half-wave dipole presents $Z_{\text{in}} = 73 + j42.5 \Omega$. Find $|\Gamma|$ and VSWR on the same line.

$$\begin{aligned}|\Gamma| &= \frac{\sqrt{23^2 + 42.5^2}}{\sqrt{123^2 + 42.5^2}} = \frac{48.3}{130.1} \approx 0.371 \\ \text{VSWR} &= \frac{1.371}{0.629} \approx 2.18\end{aligned}$$

$$|\Gamma| = \approx 0.371$$

$$\text{VSWR} = \approx 2.18$$

- (c) Compare (a) and (b): in one sentence, what did trimming to resonance buy you, and why?

Trimming killed the $+j42.5 \Omega$ of reactance, dropping VSWR from ≈ 2.2 to 1.4 — the reactance, not the resistance, was doing most of the damage.

- (d) A third dipole on the same 50 Ω line measures VSWR = 1.5, and you know it is purely resistive at that frequency. What two real Z_{in} are consistent with that reading? State what a VSWR measurement alone can and cannot tell you.

$$Z_{\text{in}} = 75 \text{ or } 33.3 \Omega$$

$$Z_{\text{in}} = 50 \cdot \frac{1.5}{1} = 75 \Omega \quad \text{or} \quad Z_{\text{in}} = \frac{50}{1.5} = 33.3 \Omega$$

VSWR is built from $|\Gamma|$ alone, so it reports the *magnitude* of the mismatch and nothing about its phase — it cannot tell you which side of Z_0 you are on, or how much of the mismatch is reactive. That is what a Smith chart, or a complex Γ measurement, is for.

3. **Quarter-wave transformer.** A resonant antenna presents a real input impedance $R_L = 36 \, \Omega$. You want to match it to a $50 \, \Omega$ feed line with a quarter-wave transformer.

- (a) What characteristic impedance Z_1 must the $\lambda/4$ section have?

$$Z_1 = \sqrt{Z_0 R_L} = \sqrt{(50)(36)} = \sqrt{1800} \approx 42.4 \, \Omega$$

$$Z_1 = \boxed{\approx 42.4 \, \Omega}$$

- (b) What is Γ at the design frequency?

The transformer makes $Z_1^2/R_L = 1800/36 = 50 \, \Omega = Z_0$, so $\Gamma = 0$.

- (c) In one sentence, what happens to the match off the design frequency, and why?

The section is $\lambda/4$ only at the design frequency; off frequency its electrical length is no longer 90° , the transformation Z_1^2/R_L no longer holds, and $|\Gamma|$ climbs — the match is narrowband.

- (d) The antenna in this problem is purely resistive. Explain in one or two sentences why a quarter-wave transformer is the wrong tool the moment Z_{in} has a reactive part.

A $\lambda/4$ section transforms R_L to Z_1^2/R_L — a *real* number into a *real* number. Hand it a complex load and the transformed impedance is still complex, so $\Gamma \neq 0$ no matter what Z_1 you pick. You must first cancel the reactance (or move to a matching topology that handles both parts at once, which is Question 4).

4. **L-match design.** A compact antenna presents $Z_{\text{in}} = 25 - j40 \, \Omega$ at $f = 1.5\text{GHz}$. You must match it to a $50 \, \Omega$ line with lumped elements. Work the match in two moves: *cancel the reactance*, then *transform the resistance*.

- (a) Find $|\Gamma|$ and VSWR for the raw, unmatched antenna.

$$\Gamma = \frac{(25 - j40) - 50}{(25 - j40) + 50} = \frac{-25 - j40}{75 - j40}$$

$$|\Gamma| = \frac{\sqrt{25^2 + 40^2}}{\sqrt{75^2 + 40^2}} = \frac{47.2}{85.0} \approx 0.555$$

$$\text{VSWR} = \frac{1.555}{0.445} \approx 3.49$$

$$|\Gamma| = \approx 0.555$$

$$\text{VSWR} = \approx 3.49$$

- (b) **Move 1.** What series reactance cancels the load reactance, and what component value does it correspond to at 1.5GHz?

Cancel $-j40 \, \Omega$ with $+j40 \, \Omega$ in series — an inductor.

$$\omega = 2\pi(1.5 \times 10^9) = 9.425 \times 10^9 \text{ rad/s}$$

$$L_1 = \frac{40}{9.425 \times 10^9} = 4.24 \text{ nH}$$

$$X_1 = +j40 \, \Omega$$

$$L_1 = 4.24 \text{ nH}$$

The load now looks like a plain $25 \, \Omega$ resistor.

- (c) **Move 2.** With $R_L = 25 \, \Omega$ real, design the L-network that transforms it to $50 \, \Omega$. Use $Q = \sqrt{Z_0/R_L - 1}$, series $X_s = QR_L$ on the load side and shunt $X_p = Z_0/Q$ on the line side. Give both reactances and both component values, and combine the two series inductors.

$$Q = \sqrt{\frac{50}{25} - 1} = 1$$

$$X_s = QR_L = 25 \, \Omega \text{ (series } L)$$

$$L_2 = \frac{25}{9.425 \times 10^9} = 2.65 \text{ nH}$$

$$X_p = \frac{Z_0}{Q} = 50 \, \Omega \text{ (shunt } C)$$

$$C = \frac{1}{\omega X_p} = \frac{1}{(9.425 \times 10^9)(50)} = 2.12 \text{ pF}$$

$$L_{\text{tot}} = 6.9 \text{ nH}$$

$$C = 2.12 \text{ pF}$$

The two series inductors merge: $L_1 + L_2 = 6.9 \text{ nH}$ ($+j65 \, \Omega$). Check: $25 - j40 + j65 = 25 + j25$, whose admittance is $0.02 - j0.02 \text{ S}$; the shunt capacitor adds $+j0.02 \text{ S}$, leaving $0.02 \text{ S} = 50 \, \Omega$ and $\Gamma = 0$.

- (d) The loaded Q of this match came out at 1. Compare the bandwidth and the practicality of this L-match against the $\lambda/4$ transformer of Question 3, and say which you would build for a 1.5GHz handheld radio.

A matching network's fractional bandwidth goes roughly as $1/Q$, so $Q = 1$ is about as broad-band as a two-element match gets — a 2:1 impedance ratio is a gentle transformation. A larger ratio would force Q up and the bandwidth down; that is the fundamental cost of matching, not a property of this topology. Against the $\lambda/4$ transformer: the transformer needs a *real* load and a physical quarter wavelength of line (5 cm at 1.5GHz), while the L-match swallows the reactance directly and occupies two 0402 parts. **Build the L-match** in a handheld — board area and the complex load both argue for it; save the $\lambda/4$ transformer for a printed feed where the line is free anyway.

5. **Mismatch that kills the amplifier.** A power amplifier (PA) delivers a forward power of $P_{\text{fwd}} = +40$ dBm toward a transmit antenna. A shunt protection diode at the PA output fails catastrophically if it must dissipate more than $P_{\text{max}} = +30$ dBm. Model *all* of the reflected power as landing on the diode, so $P_{\text{ref}} = |\Gamma|^2 P_{\text{fwd}}$.

- (a) Convert P_{fwd} and P_{max} to watts.

$$P_{\text{fwd}} = 10^{(40-30)/10} \text{ W} = 10 \text{ W}$$

$$P_{\text{max}} = 10^{(30-30)/10} \text{ W} = 1 \text{ W}$$

$$P_{\text{fwd}} = \boxed{10 \text{ W}}$$

$$P_{\text{max}} = \boxed{1 \text{ W}}$$

- (b) Find the largest $|\Gamma|$ the system can tolerate before the diode is destroyed.

$$|\Gamma|_{\text{max}} = \sqrt{\frac{P_{\text{max}}}{P_{\text{fwd}}}} = \sqrt{0.1} \approx 0.316$$

$$|\Gamma|_{\text{max}} = \boxed{\approx 0.316}$$

- (c) Convert to a VSWR limit and a return-loss limit, and state the datasheet rule that follows.

$$\text{VSWR}_{\text{max}} = \frac{1.316}{0.684} \approx 1.93$$

$$\text{RL}_{\text{min}} = -10 \log_{10}(0.1) = 10 \text{ dB}$$

Rule: keep $\text{VSWR} \leq 1.9$ (return loss ≥ 10 dB); reflected power must stay at least 10 dB below forward power.

$$\text{VSWR}_{\text{max}} =$$

$$\boxed{\approx 1.93}$$

$$\text{RL}_{\text{min}} = \boxed{10 \text{ dB}}$$

- (d) In one sentence: how does a circulator or isolator between the PA and antenna change this picture?

It routes the reflected wave into a matched dump-port load instead of back into the PA, so the diode no longer sees it — the antenna can then run at much higher VSWR (paid for by insertion loss, size, and bandwidth).

6. Baluns.

- (a) In one or two sentences, explain why feeding a dipole *directly* with coax (no balun) distorts the pattern.

Coax is unbalanced, so the two arms present unequal impedances to it. The imbalance drives a common-mode current on the *outside* of the shield; that shield current radiates, so the feed line becomes part of the antenna and skews the pattern.

- (b) You must feed a folded dipole ($Z_{\text{in}} \approx 292 \Omega$) with 75Ω coax. Which balun would you choose, and what does it do?

A 4:1 (half-wave) balun: it balances the feed *and* transforms impedance 4:1, taking 292Ω down to $\approx 73 \Omega$ — a good match to 75Ω coax.

- (c) You feed a straight resonant dipole ($\approx 70 \Omega$) with 50Ω coax. Which balun would you choose, and why is it a *different* choice than (b)?

A 1:1 current (choke) balun. The 70Ω dipole already matches 50Ω well ($\text{VSWR} \approx 1.4$), so no impedance transformation is wanted — you only need to choke off the shield current. A 4:1 balun here would ruin the match.

Documentation: _____